

晶体管的分类:

BJT:(双极晶体管) $\begin{cases} \text{PNP} \\ \text{NPN} \end{cases}$

1

FET:(场效应晶体管) $\begin{cases} \text{JFET} \\ \text{MOSFET} \end{cases}$

2

BJT

BJT 在 1948 年于贝尔实验室发明, 主要作用是放大和当作开关.
BJT 可以视为由两个共有一个区域的 PN 结构成, 两边分别是
Emiiter(发射极),Collector(集电极)和基级(Base).

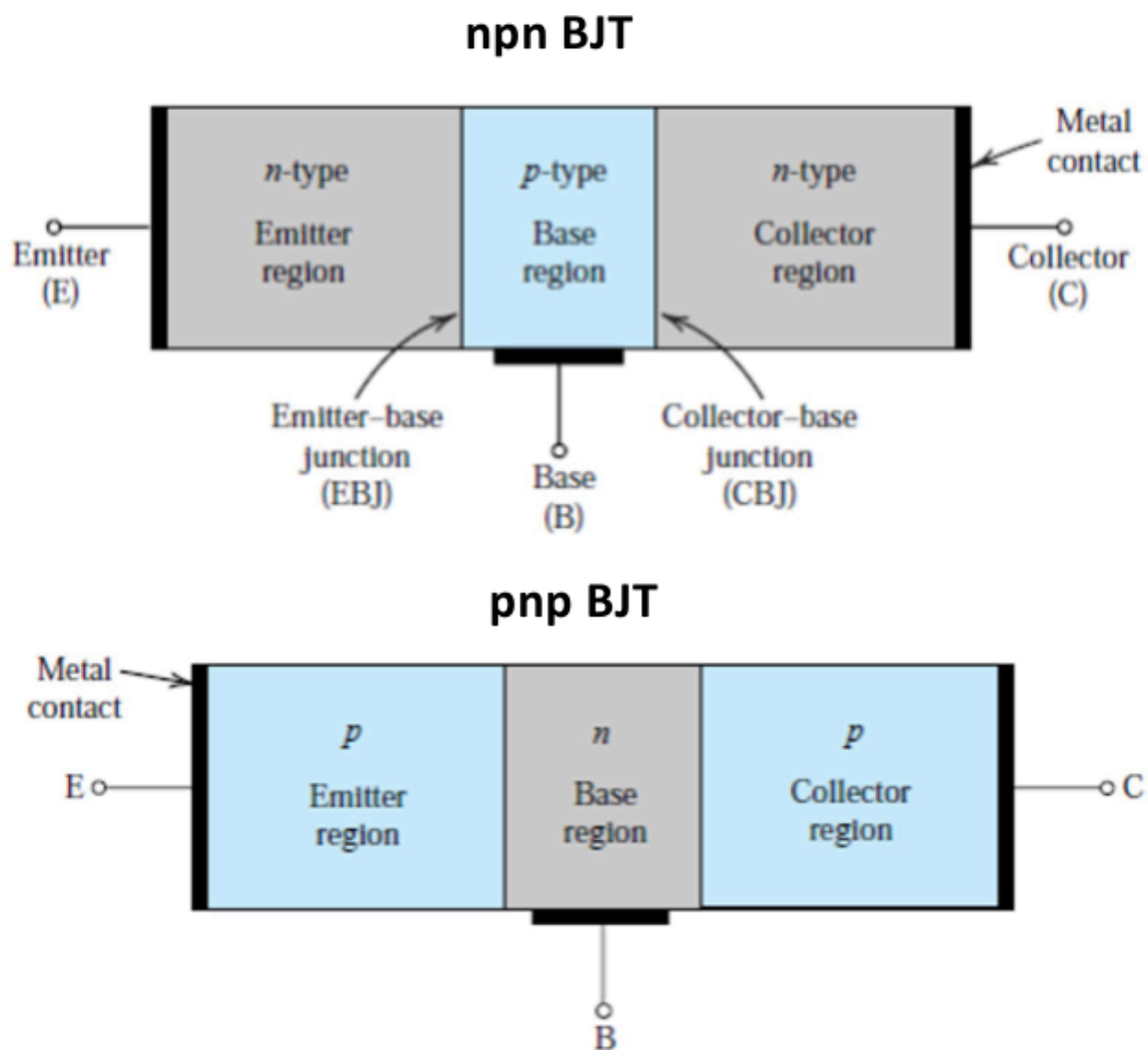


Figure 1: BJT 的结构

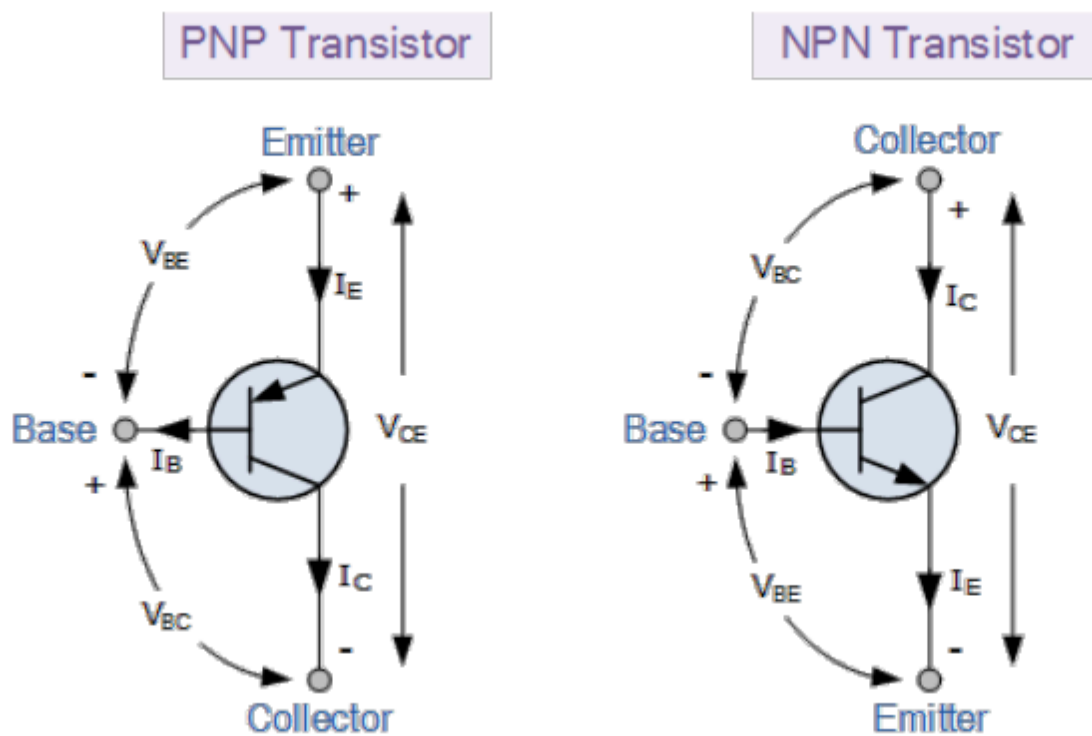


Figure 2: NPN:从 C 到 E,PNP:从 E 到 C;箭头的一端始终是 E 极

BJT 的工作模式

由 V_{BC} 和 V_{BE} 决定,组合起来是有四种?

 


Figure 3: 四种工作模式

放大区(Forward active)

- 条件: $V_{BE} > V_t \approx 0.7V, V_{CB} > 0$
- 电流放大: $I_C = \beta I_B = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$
 - $I_S = A_E q \frac{D_B}{W_B} \frac{n_{ib}^2}{N_B}$
 - D_B : 中间 P 区 少子(电子)的 diffusion 常数
 - A_E : 发射极面积
 - W_B : 基极的宽度
 - n_{ib} : 基级的本征浓度
- 对于 NPN 管, Base 和 Collector 是反向偏置的, I_C 基本不受到这个电压的影响

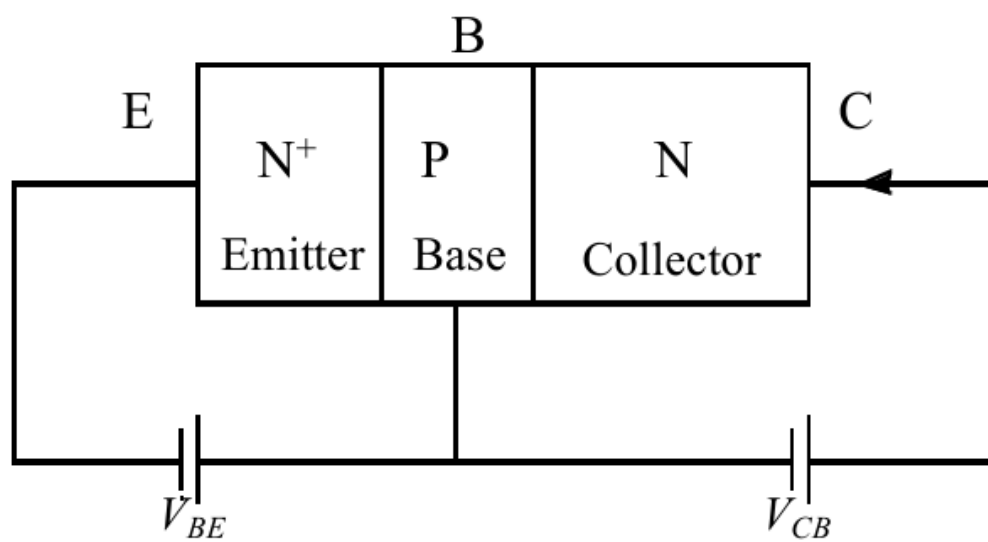


Figure 4: 放大 qu


 


Figure 5: 以 V_{CE} 为轴

 

12

Figure 6: 对于 Common Emitter, 随着 V_{CE} 增加从饱和区到放大区再到击穿区

关于电流增益(以 npn 为例子)

$$I_C = \beta I_B \quad 3$$

$$I_E = I_B + I_C \quad 4$$

$$\frac{I_C}{I_E} = \alpha = \frac{\beta}{\beta + 1} \text{ base transport factor} \quad 5$$

$$\beta_F = \frac{G_E}{G_B} = \frac{D_B W_E N_E n_{iB}^2}{D_E W_B N_B n_{iE}^2}$$

Figure 7: 用物理公式计算

BJT 的耗能

$$P = V_{BE} I_B + V_{CE} I_C \quad 6$$

基级宽度调制效应(Base-Width Modulation)

会导致在放大区, 随着 V_{CE} 的增大, I_C 也增大的效应

 


Figure 8: 基极宽度调制效应

$$I_C = \beta I_B \left(1 + \frac{V_{CE}}{V_A} \right)$$

7

 


Figure 9: 随着 V_{CE} 增加, 集电极和基极之间的耗尽层会增大

如何减小这种效应?

- 增加基极宽度
- 增加基极的参杂浓度(concentration)
- 减少集电极参杂浓度

这种效应又叫做:Early effect(Early 是人名)

BJT 的发射效率(emitter efficiency)

$$\gamma = \frac{I_E - I_B}{I_E} = \frac{I_C}{I_C + I_B}$$

8

JFET(Junction field transistor,场效应晶体管)

 


Figure 10: JFET 也有三个极(漏级,源极还有栅极)

是一种控制电压的器件(BJT 用于控制电流)

 


Figure 11: n 沟道 JFET 的结构

pinch-off voltage(夹断电压)

随着 V_{DS} 的增加, Drain 极的两个耗尽区会逐渐接近, 直到挨到一起, 这个节点的电压 是夹断电压, 夹断了之后, I_D 不随着 V_{DS} 而增加

 


Figure 12: JFET 的原理

比如沟道是 n 型的,那么其中的电子会被迅速拉入 D, 这个过程收到 V_{DS} 和 v_{GS} 的限制

在饱和区, I_D 满足 $I_D = \frac{V_p}{R_{AP}}$, 和从 A 到 P 的沟道电阻有关(S 接地)

 


Figure 13: 决定 p 的位置的重要关系 $V_{GP} = -V_p$

$I_D = \frac{V_{DS}}{R_{AB}}$, 在饱和区, 增加 V_{DS} 由于 PN-结的效应, R_{AB} 也增加了, 最终电流不会随着 V_{DS} 线性增加了

V_{GS} 的影响(之前的都是 G 和 S 一起接地的情况)

加了正的 V_{GS} , 一开始就扩展了耗尽区的厚度, 达到饱和区跟容易了

 


Figure 14: 加了 V_{GS}

新的饱和区条件: $V_{DS} = V_{GS} + V_p$

还是满足: $V_{GP} = -V_p$

V_{GS} Turn-off 的情况

$$V_{GS} = -V_p$$

9

$V_{DS} = 0$ 就完全夹断了, 完全成了耗尽层, 加上 V_{DS} 也只能由热激发的电子导电, 这个电流非常小

 


Figure 15: Turn off

JFET 的电流电压特征

 


Figure 16: V_{DS} 是常数, 由 V_{GS} 控制 I_{DS}

饱和区

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P} \right)^2 \quad 10$$

I_{DSS} 指的是 $V_{GS} = 0$ 的时候的 I_D

线性区(欧姆区)

$$I_D = k \cdot V_{DS} \quad 11$$

k 由 V_{GS} 和沟道常数等因素决定

JFET Commons Source Amplifier—用 JFET 构造放大器
asgow

 


Figure 17: 共源放大器

直流偏置 $V_{GG} < 0$, 上面加一个交流小信号,

$$g_m = \frac{i_d(i_d \text{ 的微小变化})}{v_{gs}(v_{gs} \text{ 的微小变化})} \quad 12$$

对 Equation 10 求 $\frac{\partial I_D}{\partial V_p} = \frac{2I_{DSS}}{V_p} \left(1 + \frac{V_{GS}}{V_p} \right) = \left(2\sqrt{\frac{I_{DSS} I_{DS}}{V_p}} \right)$

$$A_v = -g_m R_D \quad 13$$

, 由于非线性性质, 放大较大的信号的时候增益会比较低

MOSFET

 


Figure 18: 电容器连接负极的换成了 p 型半导体

会在 p 型半导体表面形成一个反转层, 然后是耗尽区, 使得反转层电子浓度和 p 型本体空穴浓度相等的电压就是 V_t .

 


Figure 19: n 沟道 MOSFET, S 和 D 极是高浓度参杂的

$V_{GS} > V_t$ 的话, 会形成反转层使得 S 和 D 之前能够导通, 再加上一个 V_{DS} 就能形成电流 $I_D = \frac{v_{DS}}{R_n}$


 


Figure 20: $V_{GS} > V_t$

 

Enhancement MOS

Figure 21: 增加 V_{DS} , 沟道又会出现缩小直到饱和的效应

饱和条件: $V_{DS} \geq V_{GS} - V_{th}$

 


Figure 22: 饱和区电流主要由 V_{GS} 决定

传输公式

线性区($V_{GS} > V_{th}, V_{DS} < V_{GS} - V_t$)

$$I_D = k'(V_{GS} - V_{th})V_{DS} - \frac{1}{2}k'V_{DS}^2$$

$$K = \frac{Z \mu_e \varepsilon}{2L t_{\text{ox}}}$$

Figure 23: $k' = \frac{1}{2}k$. Z 是 MOSFET 的宽度, L 是沟道长度, μ_e 是电子迁移率, $\frac{\varepsilon}{t_{\text{ox}}}$ 是氧化层电容

饱和区

$$I_D = \frac{1}{2}k'(V_{\text{GS}} - V_{\text{th}})(1 + \lambda V_{\text{DS}}) \quad 15$$


PMOS

- 线性区: $V_{\text{SG}} > |V_{\text{th}}|$, $V_{\text{SD}} < V_{\text{SG}} - |V_{\text{th}}|$, $I_D = k'[(V_{\text{SG}} - |V_{\text{th}}|V_{\text{SD}}) - \frac{1}{2}V_{\text{SD}}^2]$
- 饱和区: $I_D = \frac{1}{2}k'(V_{\text{SG}} - |V_{\text{th}}|)^2$

Enhancement MOSFET in SATURATION REGION

$$I_{\text{DS}} = K(V_{\text{GS}} - V_{\text{th}})^2(1 + \lambda V_{\text{DS}})$$

 Where λ is the channel-length modulation parameter, which is a constant that is typically 0.01 V^{-1} . It can be determined by extending I_D vs V_{DS} lines and finding the intersect at $-V_{\text{DS}}$



$$V_{\text{ov}} = V_{\text{GS}} - V_{\text{th}} (\text{override voltage})$$

$$g_m = k' V_{ov} = 2 \frac{I_D}{V_{ov}}$$

17

真空介电常数: $\epsilon_0 = 8.85 \times 10^{-12} F/m$

Depletion MOSFET(一种和增强型 MOSFET 不一样的设备)

$V_{GS} = 0$ 的时候, 就已经形成了沟道, 不需要大于 V_t ,

 


Figure 24: 耗尽型 MOSFET

它有两种模式

- 耗尽模式 $V_{GS} < 0$, 只需要更小的 V_{DS} 就可以达到饱和
- 增强模式 $V_{GS} > 0$, 需要更大的 V_{DS} 才能达到饱和

MOSFET 反向器

 


Figure 25: 简单 MOSFET 反向器

, 再输出为低电平的时候有直流电流, 所以这种门耗能大

COMS(Complementary MOS, 互补 MOS)

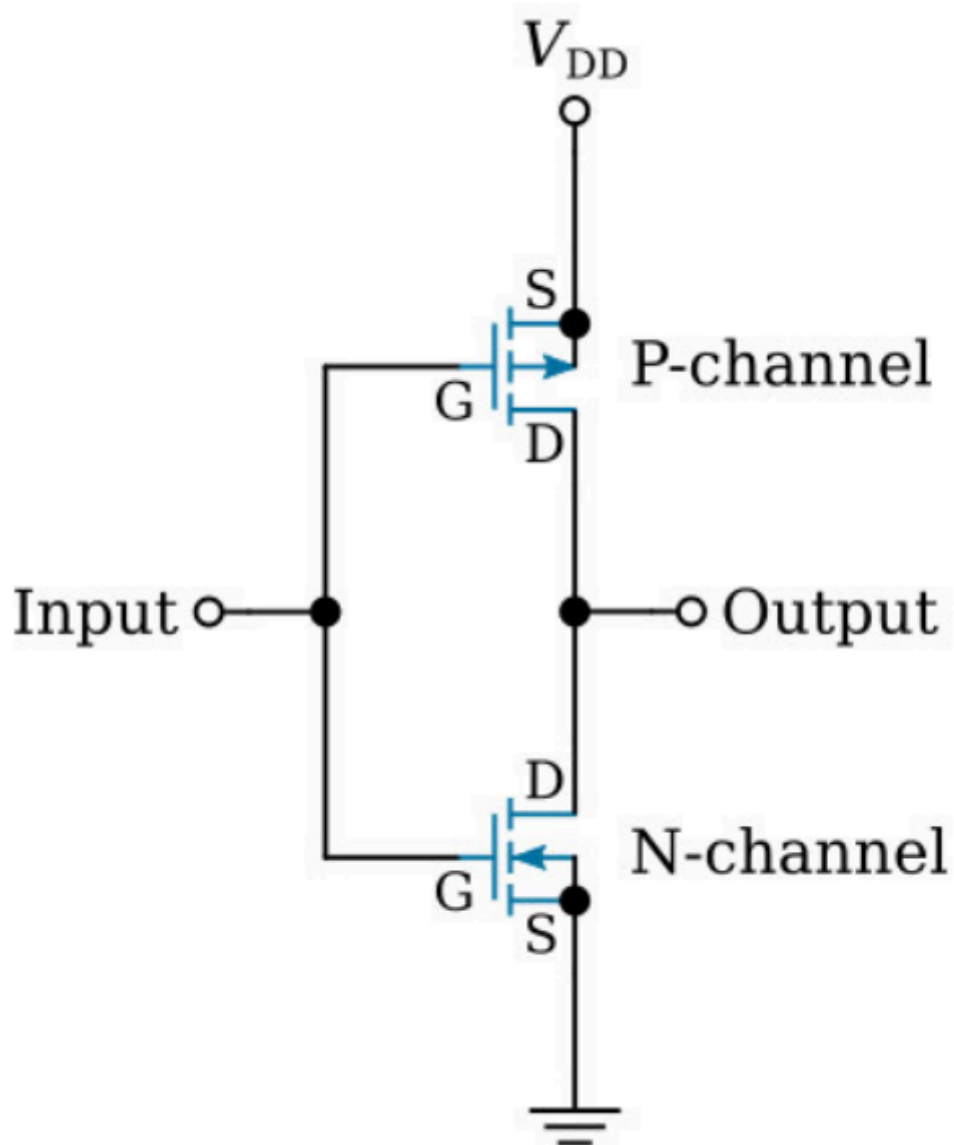


Figure 26: CMOS 的反向器的结构,没有什么电流通过

 


Figure 27: CMOS NAND ĩ

Appendix

****Given Data:****

- Gate width: $(Z = 150\text{ }\mu\text{m} = 150 \times 10^{-6}\text{ m})$
- Channel length: $(L = 10\text{ }\mu\text{m} = 10 \times 10^{-6}\text{ m})$
- Oxide thickness: $(t_{\text{ox}} = 500\text{ Å} = 500 \times 10^{-10}\text{ m} = 5 \times 10^{-8}\text{ m})$
- Electron mobility: $(\mu_e = 700\text{ cm}^2/\text{V}\cdot\text{s} = 700 \times 10^{-4}\text{ m}^2/\text{V}\cdot\text{s} = 0.07\text{ m}^2/\text{V}\cdot\text{s})$
- Threshold voltage: $(V_{\text{th}} = 2\text{ V})$
- Gate-source voltage: $(V_{\text{GS}} = 5\text{ V})$
- Drain-source voltage: $(V_{\text{DS}} = 5\text{ V})$
- Channel-length modulation parameter: $(\lambda = 0.01)$

The relative permittivity of SiO_2 : $(\epsilon_r = 3.9)$

Permittivity of free space: $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

****Step-by-step Solution:****

(a) Calculate the drain current I_D

****1. Compute the oxide capacitance per unit area**

C_{ox} :

[

$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$, where $\epsilon_{ox} = \epsilon_0 \epsilon_r$.

]

[

$\epsilon_{ox} = 8.85 \times 10^{-12} \times 3.9 = 3.4515 \times 10^{-11} \text{ F/m}$.

]

[

$C_{ox} = \frac{3.4515 \times 10^{-11}}{5 \times 10^{-8}} = \frac{3.4515 \times 10^{-11}}{5 \times 10^{-8}} = 6.9 \times 10^{-4} \text{ F/m}^2$.

]

****2. Aspect ratio Z/L :**

[

$\frac{Z}{L} = \frac{150 \times 10^{-6}}{10 \times 10^{-6}} = 15$.

]

****3. Overdrive voltage $V_{OV} = V_{GS} - V_{th}$:**

[

$V_{OV} = 5 \text{ V} - 2 \text{ V} = 3 \text{ V}$.

]

****4. MOSFET saturation current without channel-length modulation:**

In saturation (assuming $V_{DS} > V_{OV}$), which is true since $5 \text{ V} > 3 \text{ V}$):

[

$$I_{D0} = \frac{1}{2} \mu_e C_{ox} \frac{Z}{L} (V_{0V})^2.$$

Plugging in numbers:

$$I_{D0} = \frac{1}{2} (0.07) (6.9 \times 10^{-4}) (15) (3^2).$$

First, calculate the product $(\mu_e C_{ox} \frac{Z}{L})$:

$$\mu_e C_{ox} \frac{Z}{L} = 0.07 \times 6.9 \times 10^{-4} \times 15.$$

$$6.9 \times 10^{-4} \times 15 = 1.035 \times 10^{-2}.$$

$$0.07 \times 1.035 \times 10^{-2} = 7.245 \times 10^{-4}.$$

Now multiply by $((V_{0V})^2 = 9)$:

$$7.245 \times 10^{-4} \times 9 = 6.5205 \times 10^{-3}.$$

Then multiply by $(1/2)$:

$$I_{D0} = \frac{6.5205 \times 10^{-3}}{2} = 3.26025 \times 10^{-3} \text{ A} = 3.26 \text{ mA}.$$

****5. Include channel-length modulation:****

The current with channel-length modulation:

$$I_D = I_{D0} (1 + \lambda V_{DS}) = 3.26025 \times 10^{-3} (1 + 0.01 \times 5).$$

$$I_D =$$

$$1 + 0.01 \times 5 = 1 + 0.05 = 1.05.$$

\]

\[

$$I_D = 3.26025 \times 10^{-3} \times 1.05 \approx 3.423 \times 10^{-3} \text{ A} = 3.42 \text{ mA}.$$

\]

****Answer for (a):****

\[

$$I_D \approx 3.42 \text{ mA}.$$

\]

(b) Small-signal voltage gain with a 2.2 kΩ load

When the NMOS is used as a common-source amplifier with a resistor (R_D) in the drain, the small-signal voltage gain is approximately:

\[

$$A_v \approx -g_m R_D.$$

\]

****1. Compute (g_m) :**

For a MOSFET in saturation,

\[

$$g_m = \frac{2 I_D}{V_{OV}}.$$

\]

We have $(I_D = 3.42 \text{ mA})$ and $(V_{OV} = 3 \text{ V})$:

\[

$$g_m = \frac{2 \times 3.42 \times 10^{-3}}{3} = \frac{6.84 \times 10^{-3}}{3} = 2.28 \times 10^{-3} \text{ S} = 2.28 \text{ mS}.$$

\]

****2. Voltage gain:**

\[

$$A_v = -g_m R_D = -(2.28 \times 10^{-3})(2200) = -5.016 \approx -5.$$

\]

So the small-signal voltage gain is about -5.

****Determining (V_{DD}) :**

We know at the operating point $(V_{DS} = 5\text{ V})$. The drain current is (3.42 mA) , and the drain resistor is $(2.2\text{ k}\Omega)$.

$$I_D R_D = 3.42 \times 10^{-3} \text{ A} \times 2200\,\Omega = 7.524\text{ V} \\ \approx 7.53\text{ V}$$

The drain voltage at Q-point is:

$$V_D = V_{DS} + V_S = 5\text{ V} + 0\text{ V} = 5\text{ V}$$

Since $(V_D = V_{DD} - I_D R_D)$:

$$5\text{ V} = V_{DD} - 7.53\text{ V} \implies V_{DD} = 12.53\text{ V}$$

If the drain supply (V_{DD}) is smaller than 12.5 V, the transistor cannot maintain $(V_{DS}=5\text{ V})$ at the chosen operating point. The transistor might move out of saturation or the Q-point will shift, resulting in a lower gain or a distorted output swing.

****Answer for (b):****

Small-signal gain (≈ -5) .

To achieve $(V_{DS}=5\text{ V})$ at the given bias current and resistor, $(V_{DD} \approx 12.5\text{ V})$

If the drain supply is smaller, the transistor may leave saturation and the gain would drop.

(c) Maximum input signal swings

We have a quiescent point at $(V_D = 5\text{ V})$ and $(V_{DD} =$

12.5 V. The MOSFET remains in saturation as long as:

$$V_{DS} \geq V_{OV} = 3 \text{ V}.$$

The drain quiescent voltage is 5 V. The minimum drain voltage to stay in saturation is 3 V. Thus, the output can swing down from 5 V to about 3 V, a 2 V downward swing.

On the positive side, the drain can go up toward V_{DD} . The maximum upwards swing is from 5 V to about 12.5 V, which is ~ 7.5 V. Thus, the negative swing is the limiting factor for symmetrical linear operation.

Since the voltage gain is about -5, a 2 V output swing corresponds to about 0.4 V input swing (because $\Delta v_{out} = A_v \Delta v_{in} \implies \Delta v_{in} = \Delta v_{out} / |A_v| = 2/5 = 0.4 \text{ V}$).

****Answer for (c):****

- Maximum negative input swing to stay in saturation is about ± 0.4 V (around the Q-point) to avoid pushing the output below 3 V.
- On the positive side, there is more headroom, but the limiting factor is the lower saturation boundary. Thus, about ± 0.4 V input signal can be cleanly amplified if a symmetrical swing is desired.

(d) Factors leading to higher voltage amplification

The voltage gain of a common-source stage is approximately:

$$A_v \approx -g_m R_{load}.$$

To increase the gain:

1. ****Increase g_m :****

- Increase the bias current I_D .
- Increase the device transconductance by using a larger W/L .

L ratio.

- Use a higher mobility transistor or reduce threshold to increase (V_{0V}) for given bias.

2. ****Increase load resistance (R_D) ****

- Use a larger resistor.
- Replace the resistor with an active load (current mirror load), increasing the effective load impedance.

3. ****Increase supply voltage (V_{DD}) ****

- Allows for larger (R_D) while maintaining the transistor in saturation, thus increasing gain.

4. ****Reduce channel-length modulation (λ) ****

- Using longer channel devices or cascoding increases the output impedance, effectively boosting gain.

****Answer for (d)****

Higher voltage amplification can be achieved by increasing transconductance (larger (I_D) , larger W/L, higher (μ_e)), increasing load resistance (or using active loads), increasing (V_{DD}) to allow higher load resistance while keeping the transistor in saturation, and reducing (λ) through device geometry or cascoding.

****Final Answers:****

- (a) $(I_D \approx 3.42 \text{ mA})$
- (b) Gain (≈ -5) , $(V_{DD} \approx 12.5 \text{ V})$. If (V_{DD}) is smaller, the transistor may leave saturation, reducing gain.
- (c) About $\pm 0.4 \text{ V}$ input swing for symmetrical undistorted output swing given the determined Q-point and gain.
- (d) Higher gain is achieved by increasing (g_m) , increasing (R_D) or using active loads, increasing (V_{DD}) , and reducing (λ)

为什么基极很窄?

- 避免载流子被复合, 提高从发射极到集电极的传输效率, 增大电流增益

